

6.2.23 Science Home Learning

We have done a lot of learning this half term about electrical circuits, what components the symbols represent and even made our own circuits. Today, you are going to explain whether or not the circuits would work. There is more learning here if you need it:

<https://www.bbc.co.uk/bitesize/topics/zcjb6yrd/articles/zdwl382>

Will these circuits work? Think about which components are needed to ensure an electric current runs through it safely to make a buzzer/ bulb/ motor work. Below write down if it works or not and why.

